
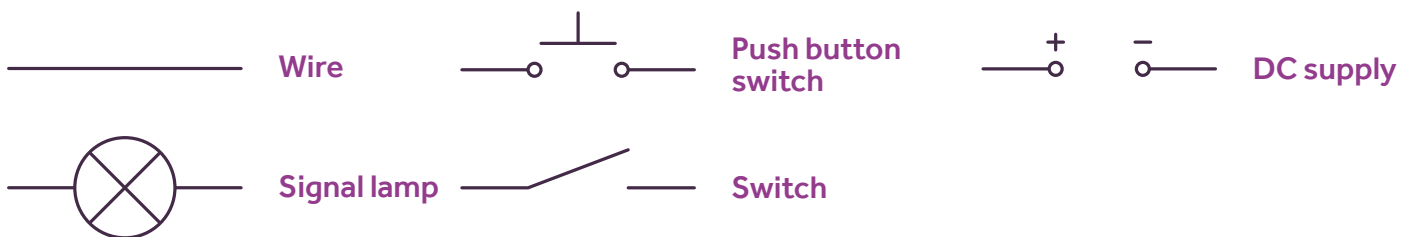


Electrics time

Powering the railway

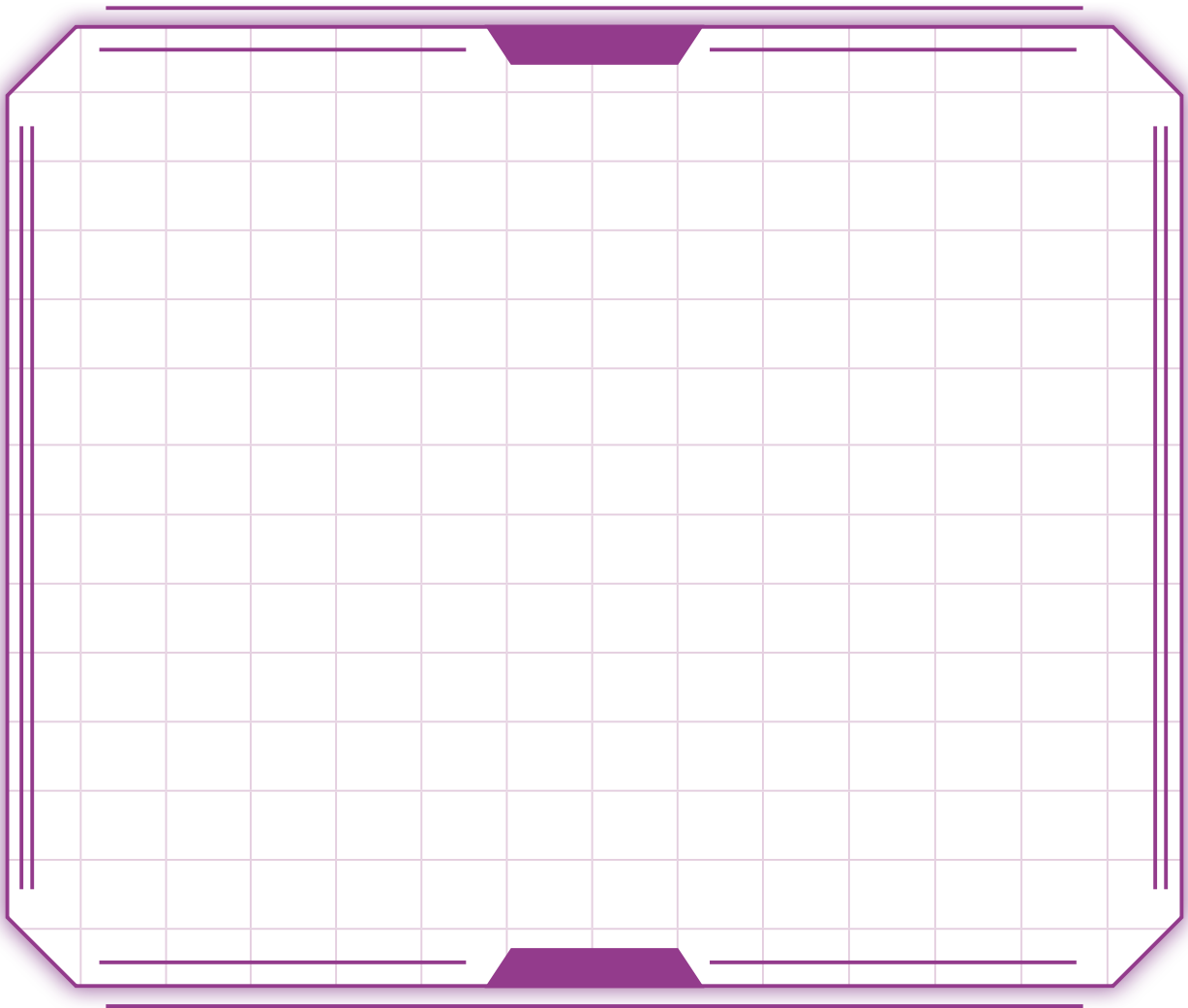Can you draw a circuit to make the signal lamp work using the elements below?



Name: _____ Age: _____ City/town: _____